



INDIAN SCHOOL AL WADI AL KABIR


Class: XI	Department: Computer Science	Date of submission:
Worksheet -3	Topic: Boolean Algebra	Note: for practice

1. Prove the Boolean Laws shown below using Truth Table.


1. $X + X'Y = X + Y$
2. $X + XY = X$
3. $X + YZ = (X + Y)(X + Z)$

2. Convert the following logic gate circuit into a Boolean expression.(Write the Boolean expression for the given circuits)


1.

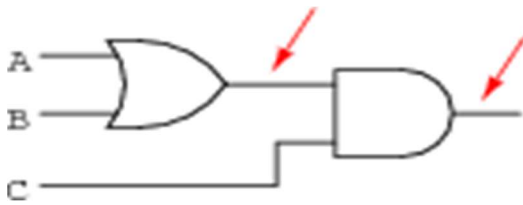

2.

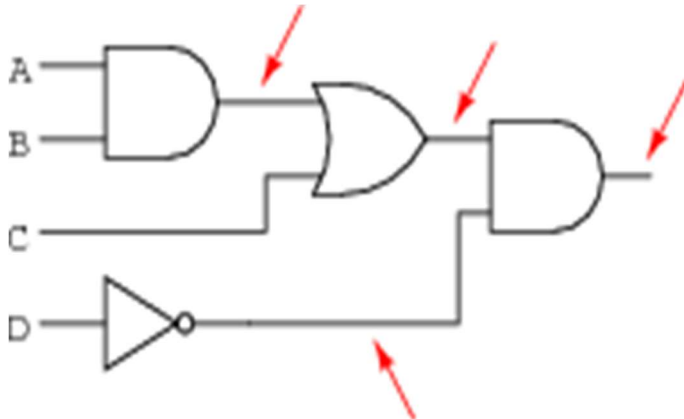

3.

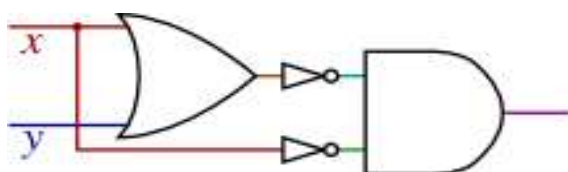


3.

1. Draw Logic circuit for $y = A.C + B.C' + A'.B.C$

2. Draw Boolean Logical Circuit from the given Boolean expression: $Q = A.B + B.C.(B+C)$
3. Draw Logic circuit for $y = A.C + B.C' + A'.B.C$
4. Draw a circuit diagram corresponding to the following Boolean Expression:
 - a) $y = A+C .B+C' . A'+B+C$
 - b) $F = A'.B.C.(A+D)'$
 - c) $F = A.B'+C'.D$
 - d) $F = (U.V')+(U'.W')$
 - e) $F = A.B + A.C' + B'.A'.C$
 - f) $F = (X+Y).(X'+Z').(Y+Z)$

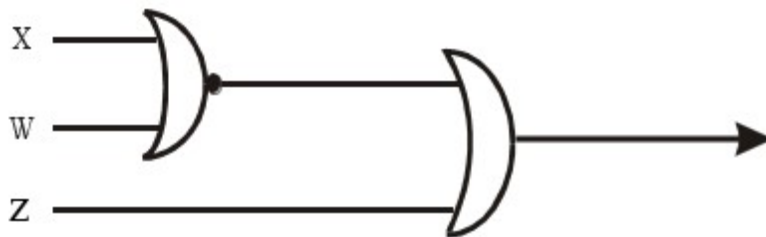4. Obtain logic expression for the following logic circuit:



5. Find the result of the following logic circuit

